

## LAB 2

### Case 1 : with only single adder


In 1 clock cycle -> load the values in Input 1 and Input 2

In 2-11 clock cycle -> Adder takes 10 clock cycles thus represented by state machine with 10 states

In 12 clock cycle -> it will provide the output

Now based on this 1 pair of Inputs takes 12 cycles to process and provide output

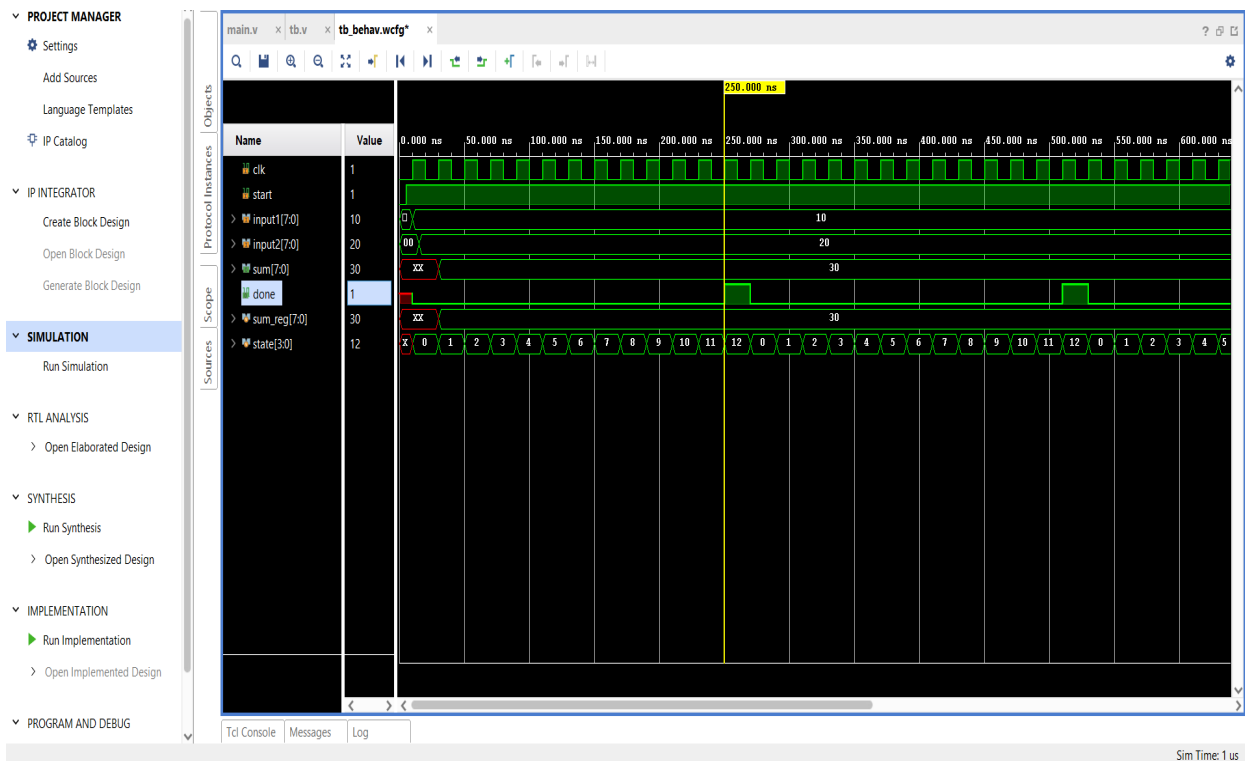Based on this for N=400 , it would take around **4800 cycles** to process and provide output .



Simulation for 1 adder

### Case 2 : with 5 adder in parallel in pipeline structure

Load Input 1 and Input 2 for Adder 1 -> (Cycle 1)

Load Input 1 and Input 2 for Adder 2 ->(Cycle 2)

Load Input 1 and Input 2 for Adder 3 ->(Cycle 3)

Load Input 1 and Input 2 for Adder 4 ->(Cycle 4)

Load Input 1 and Input 2 for Adder 5 ->(Cycle 5)

Adder 1 performs the addition -> (Cycles 2-11)


Adder 2 performs the addition -> (Cycles 3-12)

Adder 3 performs the addition -> (Cycles 4-13)

Adder 4 performs the addition -> (Cycles 5-14)

Adder 5 performs the addition ->(Cycles 6-15)

Output from Adder 1 available ->(Cycle 12)  
 Output from Adder 2 available -> (Cycle 13)  
 Output from Adder 3 available ->(Cycle 14)  
 Output from Adder 4 available -> (Cycle 15)  
 Output from Adder 5 available -> (Cycle 16)  
 Load Input 1 and Input 2 for Adder 1 ->(Cycle 17) and so on ..  
 SO based on this we get 16 cycles to get output from all the parallel 5 adders for 1 input pair  
 each parallely  
 Now in order to get for N=400  
 Total cycles required will be  $16/5 * 400$   
**1280 cycles!**

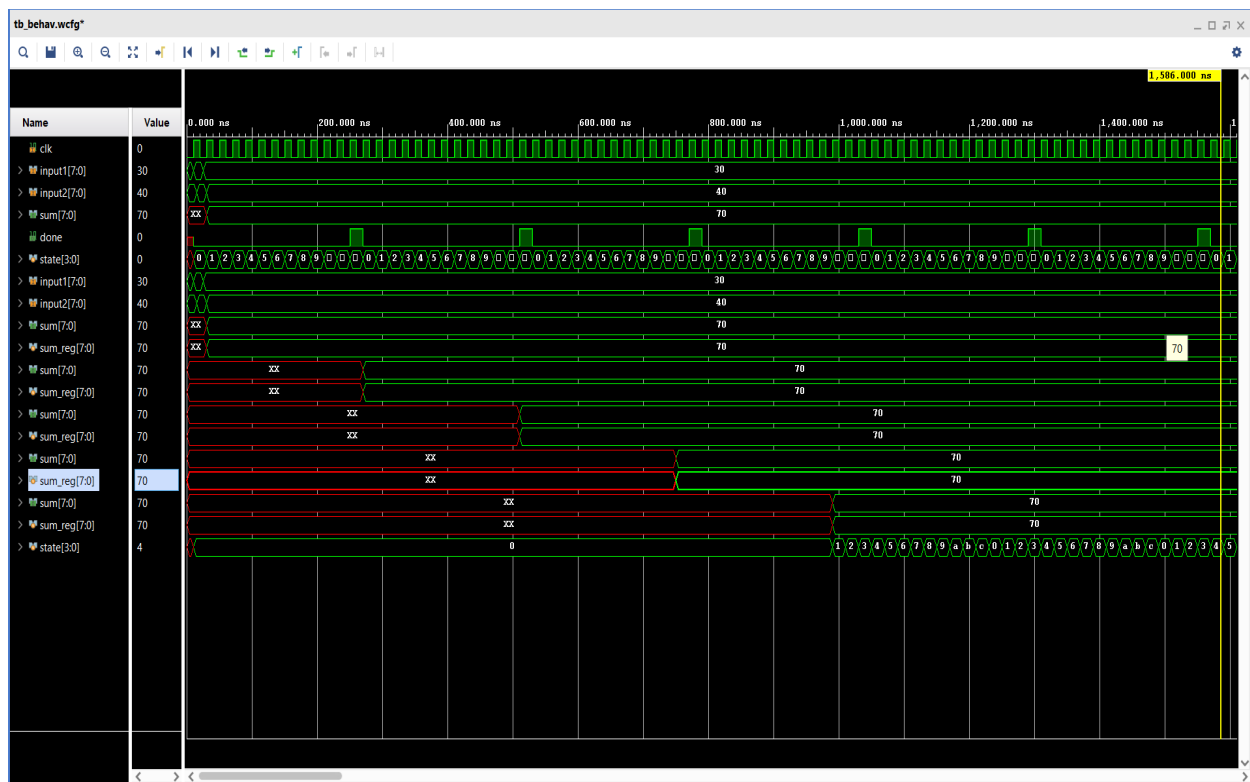

Simulation for 5 adder

